

Assignment3

Design 4-bit counter using signed magnitude representation. The following sequence has to be followed in the counter:

{-7,-6, -5,.....0.....5, 6,7 , -7

Plot the the following waveforms: a) clock and b0 bit b) clock and b1 bit.

Assume that D-flip flop and basic gates are available.